



All resistors 47K Ω .

RB 1 in Kenwood

on counter
board.

TS-120S

This can be made up using small
resistors* if RB 1 breaks.
I used small m.o. resistors.